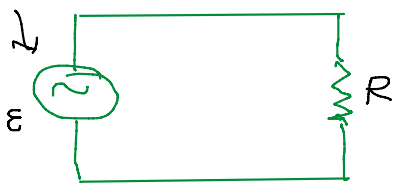


# A.C. Voltage applied to a resistor

18 July 2019 10:38

a.c. source



Ohm's law

$$V = IR \quad \text{--- (2)}$$

$$V = V_m \sin \omega t$$

$$IR = V_m \sin \omega t \quad (\text{from (1) \& (2)})$$

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

Where

$V =$  a.c. voltage

$V_m =$  voltage amplitude (or) peak voltage

$\omega =$  angular frequency

$$I = \frac{V_m \sin \omega t}{R}$$

$$I = I_m \sin \omega t$$


$$I_m \sin \omega t = \frac{V_m \sin \omega t}{R}$$

$$I_m = \frac{V_m}{R}$$

$R =$  Resistance (constant)

$V_m =$  voltage amplitude (or) peak voltage

$I_m =$  peak current

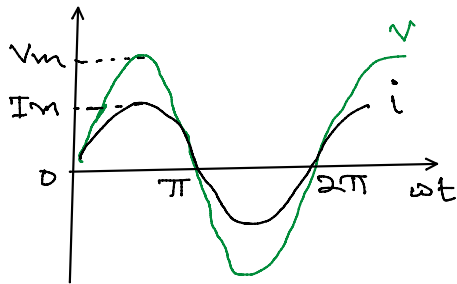

$I_m =$  peak current  
 $V_m =$  peak voltage  
 $V =$  voltage  
 $I =$  current

Joule's heating

$$H = I^2 R$$

$H =$  Heat dissipated

Power dissipated

$$P = I^2 R$$

$$P = I_m^2 \sin^2 \omega t R$$

$$P = I_m^2 R \sin^2 \omega t$$

$$\bar{P} = \langle I^2 R \rangle$$

$$\bar{P} = I_m^2 R \langle \sin^2 \omega t \rangle$$

$$I = I_m \sin \omega t$$

$\bar{P} =$  average power

$\langle \rangle =$  average of the quantity

$I_m^2 R =$  constants

$$\sin^2 \theta = \frac{(1 - \cos 2\theta)}{2}$$

$\langle 1 - \cos 2\omega t \rangle$  | NOTE  
 Average value of a  
 over a period,  $T$

$$P = I_m^2 R \left\langle \frac{1 - \cos 2\omega t}{2} \right\rangle$$

$$P = I_m^2 R \times \frac{1}{2}$$

\* 
$$P = \frac{1}{2} I_m^2 R$$

A.C. POWER

NOTE  
Average value of a function over a period, T is given by

$$\langle F(t) \rangle = \frac{1}{T} \int_0^T F(t) dt$$

$$\langle \cos 2\omega t \rangle = \frac{1}{T} \int_0^T \cos 2\omega t dt$$

$$= \frac{1}{T} \left[ \frac{\sin 2\omega t}{2\omega} \right]_0^T$$

$$\int \cos ax dx = \frac{\sin ax}{a}$$

\* 
$$P = I^2 R$$

DC Power

A.C. Power

$$I^2 R = \frac{1}{2} I_m^2 R$$

$$I^2 = \frac{I_m^2}{2}$$

Taking  $\sqrt{\quad}$  on both sides

$$\sqrt{I^2} = \sqrt{\frac{I_m^2}{2}}$$

$I_{rms}$  
$$I = \frac{I_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \times \frac{\sqrt{2}}{\sqrt{2}} = \frac{\sqrt{2} \cdot I_m}{2} = \frac{1.414 \cdot I_m}{2}$$

I or  $I_{rms}$

= effective current  
= root mean square value of current

$$I \text{ (or)} \frac{I}{rms} = 0.707 I_m$$

$$I = \sqrt{I} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

Average power (P)

$$P = \frac{1}{2} I_m^2 R = I^2 R$$

$$V = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

$$\frac{1}{2} \frac{V_m^2}{R^2} \cdot R = \frac{V^2}{R}$$

$$V^2 = \frac{V_m^2}{2}$$

$$V = \frac{V_m}{\sqrt{2}}$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$V = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

$$V_m = I_m R$$

$$\frac{V_m}{\sqrt{2}} = \frac{I_m}{\sqrt{2}} R$$

$$V = IR$$

$V$  = rms voltage  
(or)  
effective  
voltage

$$V = \frac{V_m}{\sqrt{2}}$$

$$V_m = \sqrt{2} V$$

$$V_m = 1.414 V$$

NOTE when rms voltage is 220 V, the peak voltage is given by

$$V_m = 1.414 \times 220 = \underline{\underline{311 \text{ volt}}}$$